

Q1 (Total 30 marks)

For the 2-stage amplifier shown in Figure 1, the circuit parameters are given below.

$$R_1 = 67.3 \text{ k}\Omega, R_2 = 12.7 \text{ k}\Omega, R_{C1} = 10 \text{ k}\Omega, R_{E1} = 2 \text{ k}\Omega$$

$$R_3 = 15 \text{ k}\Omega, R_4 = 45 \text{ k}\Omega, R_{E2} = 1.6 \text{ k}\Omega$$

$$R_L = 250 \Omega$$

C_1, C_2, C_3 are coupling capacitors and have very large values. C_E is an emitter bypass capacitor.

$$\beta = 120 \text{ for both transistors, } Q_1 \text{ and } Q_2, \alpha = 0.99 \text{ and } V_T = 0.026 \text{ V}$$

For this amplifier,

- (a) Draw the DC model of the circuit and calculate the Q-point parameters, I_{CQ} and V_{CEQ} for both transistors. **(14 marks)**

- (b) Draw the small signal (AC) model of the circuit and calculate the small-signal parameters, g_m and r_π for both transistors. **(6 marks)**

and calculate:

- (c) The overall small-signal gain, $A_V = v_o/v_s$. **(6 marks)**
 (d) The input resistance, R_{is} . **(1.5 marks)**
 (e) The output resistance, R_o . **(2.5 marks)**



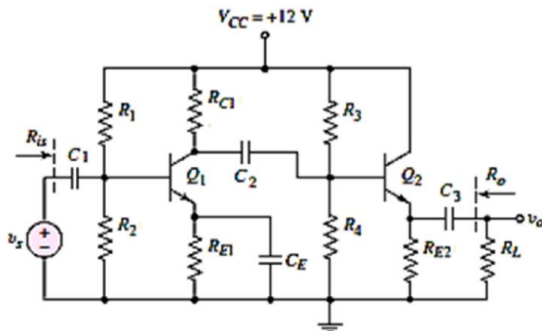


Figure 1.

a) First analysing in DC, we understand the capacitors are open sources leaving us with a first and second side amplifier.

First
Stage

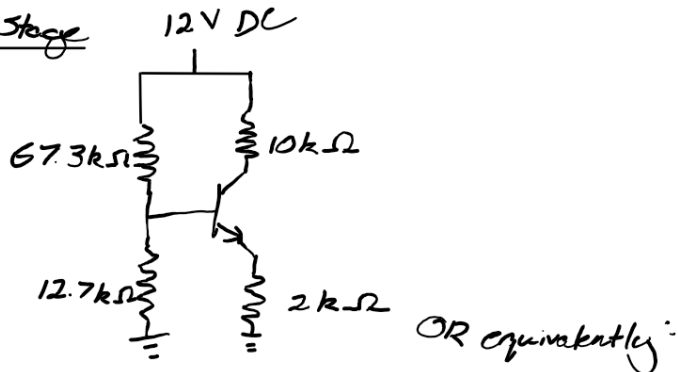

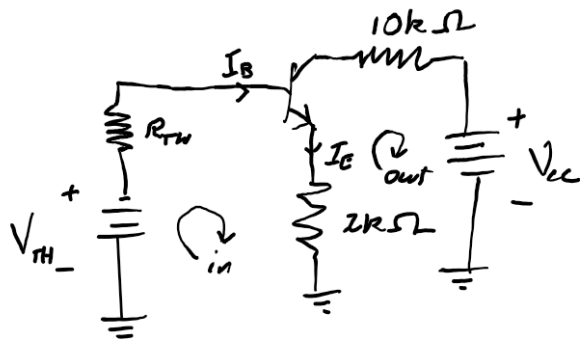

where $R_{TH} = R_1 \parallel R_2$
 $= \frac{R_1 R_2}{R_1 + R_2} = 10.68 k\Omega$

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{12.7 k\Omega}{(12.7 + 67.3) k\Omega} \times 12$$

$$= 1.905 V$$

KVL of input loop:

$$V_{TH} = R_{TH} I_B + R_E I_E + V_{BE} \quad \text{Given } I_E = (\beta + 1) I_B$$

and $\beta = 120$
 $V_{BE} = 0.7 V$

$$1.905 = 10.680 I_B + 2000 \times 121 I_B + 0.7$$

$$I_B = 4.8 \mu A$$

$$I_C = \beta I_B = 576 \mu A$$

$$\therefore I_E = 580.8 \mu A \quad (I_B + I_C)$$


KVL at output loop:

$$V_{CC} = 10000 I_C + V_{CE} + 2000 I_E$$

$$V_{CE} = 12 - 10000(576 \times 10^{-6}) - 2000(580.8 \times 10^{-6})$$

$$\approx 5.08 V$$

For the second stage:

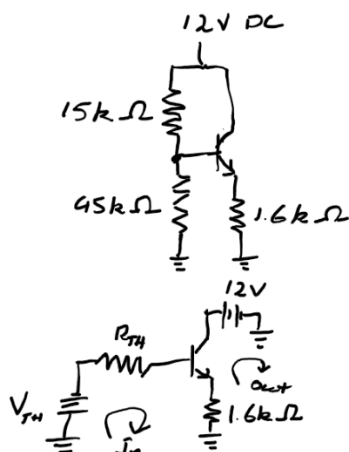

Equivalent circuit

$$R_{TH} = 15 k\Omega \parallel 45 k\Omega$$

$$= 11.25 k\Omega$$

$$V_{TH} = \frac{45 k\Omega}{(45 + 15) k\Omega} \times V_{CC}$$

$$= 9 V$$

KCL on input loop:

$$V_{TH} = R_{TH} I_B + V_{BE} + R_E I_E \quad \text{note } I_E = 121 I_B$$

$\downarrow (B+1)I_B$

$$V_{BE} = 0.7V$$

$$I_B = \frac{9 - 0.7}{11.25 \times 10^3 + 1.6 \times 10^3 (121)}$$
$$\approx 4.05 \times 10^{-5} \text{ A}$$

$$\therefore I_E = 121 I_B = 0.0049 \text{ A}$$

$$I_C = 120 I_B = 0.00486 \text{ A}$$

KCL on output loop:

$$V_{CC} = V_{CE} + R_E I_E$$
$$V_{CE} = 12 - 1600 \times 0.0049$$
$$= 4.16 \text{ V}$$

b) We know $g_m = \frac{I_C}{V_T}$

For the first transistor

$$g_{m1} = I_{CQ} / V_T$$

$$= \frac{576 \times 10^{-6}}{0.026}$$

$$= 0.022$$

$$r_{\pi 1} = \frac{\beta V_T}{I_{CQ}}$$

$$= \frac{120 \times 0.026}{576 \times 10^{-6}}$$

$$= 5416.67$$

For the second:

$$g_{m2} = I_{Q2} / V_T$$

$$= \frac{0.00486}{0.026}$$

$$= 0.19$$


$$r_{\pi2} = \frac{\beta V_T}{I_{CQ2}}$$

$$= \frac{120 \times 0.026}{0.00486}$$

$$= 641.98$$


Now drawing the diagram:

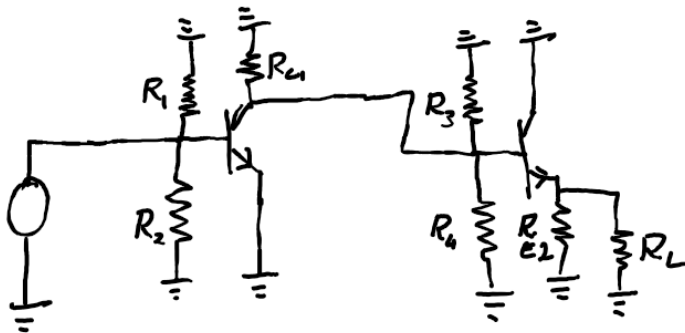
Shorting the capacitors and zeroing the DC source we find:



Now drawing the equivalent transistor diagrams:

Note that R_3 and

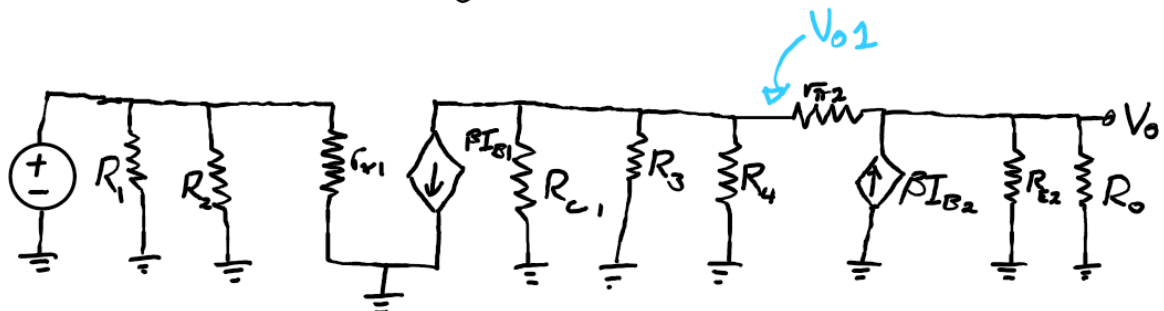

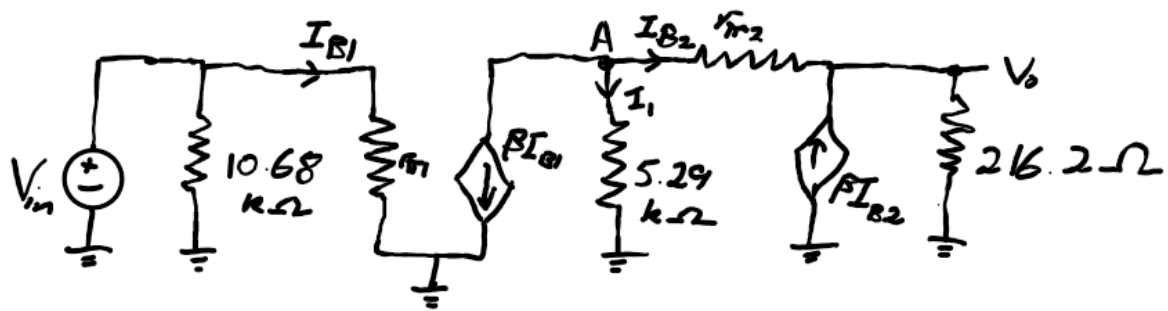

For stage 1:

For common collector

$$R_{B1} = R_1 \parallel R_2 = 10.683 \text{ k}\Omega$$

$$R'_{L1} = R_{C1} \parallel R_3 \parallel R_4 = 5.294 \text{ k}\Omega$$

$$A_{V1} = \frac{R'_{L1} \beta}{r_{\pi}} \quad \therefore A_{V1} = \frac{5.294 \times 10^3 \times 120}{5416.67} = -117.28$$

Now for second stage:

For common emitter

$$R'_{L2} = R_L \parallel R_E = 216.22 \Omega$$

$$A_{V2} = \frac{(1 + \beta) R'_{L2}}{r_{\pi} + (1 + \beta) R'_{L2}} = 0.976$$

Finally, the total gain A_v :

$$A_v = A_{v1} \times A_{v2} = -114.47$$

$$\text{Thus } V_o = -114.47 V_{in}$$

d) The total input resistance is for that of the common emitter.

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1}{\frac{1}{R_B} + \frac{1}{r_{\pi}}} \quad \begin{array}{l} R_{B1} = 10.683 \text{ k}\Omega \\ r_{\pi} = 5416.67 \Omega \end{array}$$
$$= 3945.35 \Omega$$

e) The total output resistance is for that of the common collector.

$$Z_o = \frac{V_o}{I_o} = \frac{1}{(1+\beta)(R'_S + r_{\pi}) + 1/R_E}$$

$$\text{Given } R'_S = \left(\frac{1}{R_5} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1}$$

$$R_5 = 0$$

$$r_{\pi 2} = 641.98$$

$$\beta = 120$$

$$R_E = 1600$$

$$Z_o = 6.9 \times 10^{-7} \Omega$$

Q2 (Total 30 marks)

For the Figure 2 sketch v_o versus v_{in} to scale when v_{in} changes from -10 V to +10 V. Assume that diodes are ideal. Explain possible states of the diode when v_{in} changes in the above range.


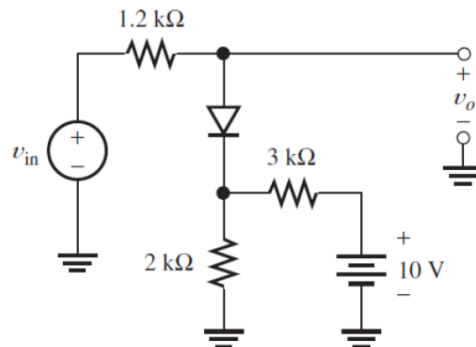


Figure 2

We must consider three cases:

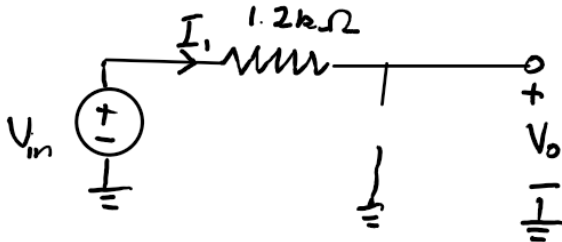Case 1, Diode reverse bias. During this state, no current flows through the diode. Thus it is an open circuit:




During this stage, $I_1 = 0$ as no ground is connected, and thus no voltage drop over the $1.2\text{ k}\Omega$ resistor.

Thus $v_o = v_{in}$

Case 2: The diode is on, but the current through it is almost 0A. As a result, v_{in} will still equal v_o , but, this will mark the first v_{in} which creates a forward bias.

$$\therefore v_{in} = v_o \quad I_1 = 0.0000\dots 1 \approx 0$$

Diode becomes a short:

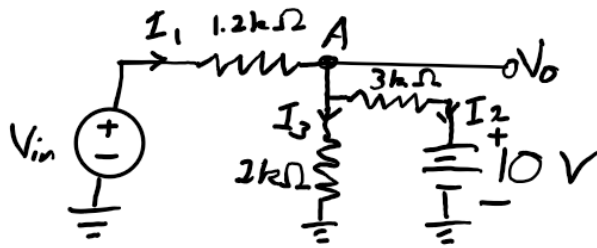

KVL: $V_{in} = 1200 I_1 + 2000 I_3 \quad (I_1 = 0)$
 $V_{in} = 2000 I_3$

$$10 + 3000 I_2 = 2000 I_3$$

Notice $I_2 + I_3 = 0 \rightarrow I_3 = -I_2$


Thus:

$$10 - 3000 I_3 = 2000 I_3$$

$$I_3 = \frac{10}{5000} = \frac{1}{500}$$

$$\therefore V_{in} = 2000 \times \frac{1}{500} = 4 \text{ V}$$

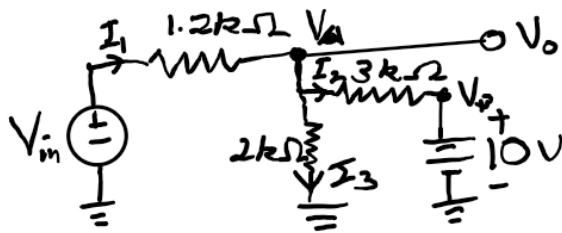Case 3: V_{in} is over 4V and thus $I_1 > 0$:



KCL at V_A :

$$I_1 = I_2 + I_3$$

$$\frac{V_{in} - V_A}{1200} = \frac{V_A - V_B}{3000} + \frac{V_A - V_G}{2000}$$

$$\frac{V_{in} - V_A}{1200} = \frac{V_A - 10}{3000} + \frac{V_A - 0}{2000}$$


$$\frac{V_{in}}{1200} = \frac{V_A}{600} - \frac{10}{3000}$$

$$V_{in} = 2V_A - 4$$

Given $V_A = V_o$ we can rearrange:

$$V_{in} + 4 = 2V_o \rightarrow V_o = \frac{1}{2}V_{in} + 2$$

Finally plotting this:

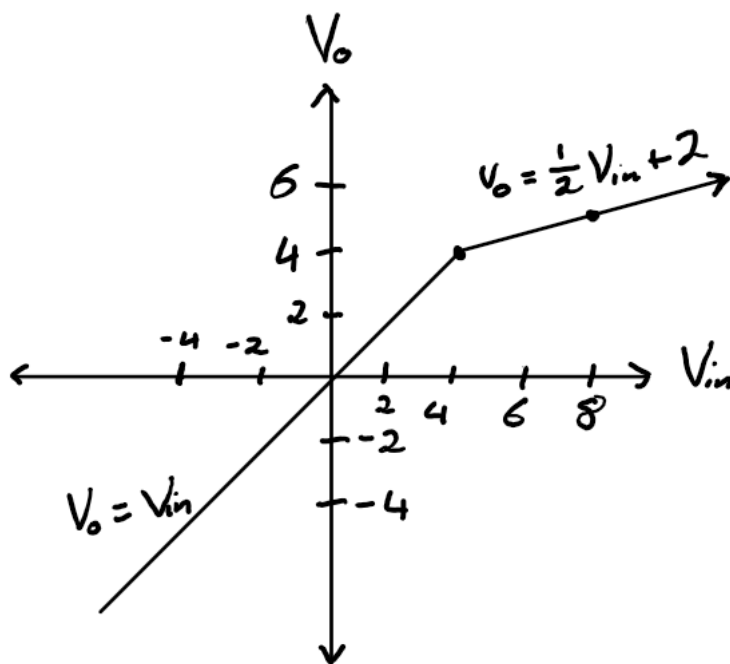

Q3 (Total 40 marks)

Figure 3 shows an equivalent circuit of a Darlington pair configuration. The transistor parameters are $\beta_1 = 120$, $\beta_2 = 80$, $V_{A1} = 80$ V and $V_{A2} = 50$ V. Assume $V_T = 0.026$ V. Draw the small signal equivalent circuit and determine the output resistance R_o for $I_{C2} = I_{Bias} = 1$ mA. (V_{A1} and V_{A2} are Early voltages, which have been discussed in Lecture 5 "Introduction to Multistage Amplifiers".)


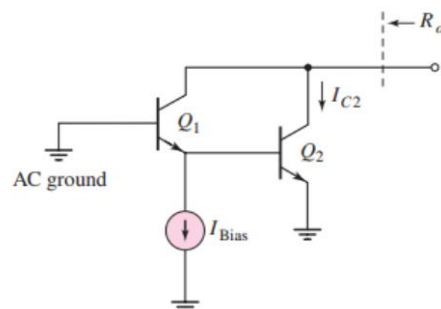


Figure 3

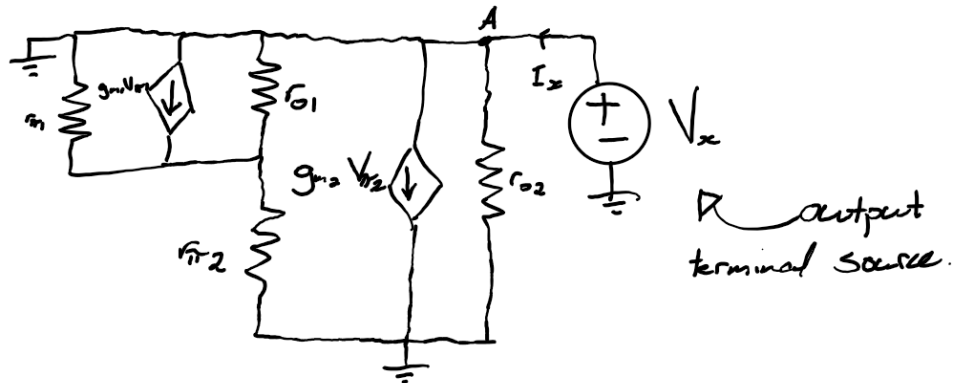Drawing the small signal equivalent circuit



Given we know $I_{C2} = I_{B_{in2}} = 1 \text{ mA}$

$$I_{C1} = \left(\frac{\beta_2 + 1}{\beta_2} \right) \left(\frac{\beta_1 + 1}{\beta_1} \right) I_{C2} \quad \begin{matrix} \beta_1 = 120 \\ \beta_2 = 80 \end{matrix}$$

$$= 1.004 \text{ mA}$$

Given $g_m = \frac{I_{CQ}}{V_T}$ and $V_T = 0.026$

$$g_{m1} = \frac{1.004 \times 10^{-3}}{0.026}$$

$$= 0.03862 \text{ A/V}$$

$$g_{m2} = \frac{1 \times 10^{-3}}{0.026}$$

$$= 0.03846 \text{ A/V}$$

And given $r_{\pi} = \frac{\beta V_T}{I_{CQ}}$

$$r_{\pi1} = \frac{120 \times 0.026}{1.004 \times 10^{-3}}$$

$$= 3.108 \text{ k}\Omega$$

$$r_{\pi2} = \frac{80 \times 0.026}{1 \times 10^{-3}}$$

$$= 2.08 \text{ k}\Omega$$

And finally:

$$r_o = \frac{V_A}{I_{CQ}}$$

$$\begin{matrix} V_{A1} = 80 \text{ V} \\ V_{A2} = 50 \text{ V} \end{matrix}$$

$$r_{o1} = 79.68 \text{ k}\Omega$$

$$r_{o2} = 50 \text{ k}\Omega$$

KCL at A:

$$I_x = \frac{V_x}{r_{o2}} + g_{m2} V_{\pi 2} + \frac{V_x - V_{\pi 2}}{r_{o1}} + g_{m1} V_{\pi 1}$$

Given we also notice $V_{\pi 1} = -V_{\pi 2}$ (KVL)

$$I_x = \frac{V_x}{r_{o2}} + g_{m2} V_{\pi 2} + \frac{V_x - V_{\pi 2}}{r_{o1}} - g_{m1} V_{\pi 2}$$

$$I_x = \left(\frac{1}{r_{o2}} + \frac{1}{r_{o1}} \right) V_x + \left(g_{m2} - \frac{1}{r_{o1}} - g_{m1} \right) V_{\pi 2} \quad (2)$$

We also know $V_{\pi 2} = I r_{\pi 2}$

using KCL to find I through $r_{\pi 2}$:

$$I_{\pi 2} = \frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + \frac{V_x - V_{\pi 2}}{r_{o1}}$$

$$\text{Thus } V_{\pi 2} = \left(\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1} V_{\pi 1} + \frac{V_x - V_{\pi 2}}{r_{o1}} \right) r_{\pi 2}$$

$$V_{\pi 2} = \frac{-V_{\pi 2}}{r_{\pi 1}} r_{\pi 2} - g_{m1} V_{\pi 2} r_{\pi 2} + \frac{V_x}{r_{o1}} r_{\pi 2} - \frac{V_{\pi 2}}{r_{o1}} r_{\pi 2}$$

$$\therefore V_{\pi 2} = \frac{V_x r_{\pi 2}}{r_{o1} \left(1 + \frac{r_{\pi 2}}{r_{\pi 1}} + r_{\pi 2} g_{m1} + \frac{r_{\pi 2}}{r_{o1}} \right)}$$

$$V_{\pi 2} = 0.00032 V_x$$

Thus substituting into (2)

$$I_x = \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) V_x + \left(g_{m2} - \frac{1}{r_{o1}} - g_{m1} \right) \times 0.00032 V_x$$

$$\text{Thus } \frac{V_x}{I_x} = R_o$$

$$= \frac{1}{\left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) + \left(g_{m2} - \frac{1}{r_{o1}} - g_{m1} \right) \times 0.00032}$$

$$= 30.7 \text{ k}\Omega$$

Thus the output impedance is $30.7 \text{ k}\Omega$