

ELEC2400 A2 – Samuel Allpass

s4803050

- (a) Assuming that $R_{C1} = R_{C2} = 10 \text{ k}\Omega$, and the internal resistance R_{EB} of the current source is infinite, calculate DC bias points (Q-points) for all the transistors in Figure 1. Classify the region of operation of each transistor as *active*, *cut-off* or *saturation*. Will your classification change if $R_{EB} = 470 \text{ k}\Omega$? You should state and justify any assumptions that you make.

a) with $V_1 = V_2 = 0 \text{ V}$ we find:
and assume Q_1 , Q_2 and Q_3 are
in the active region.

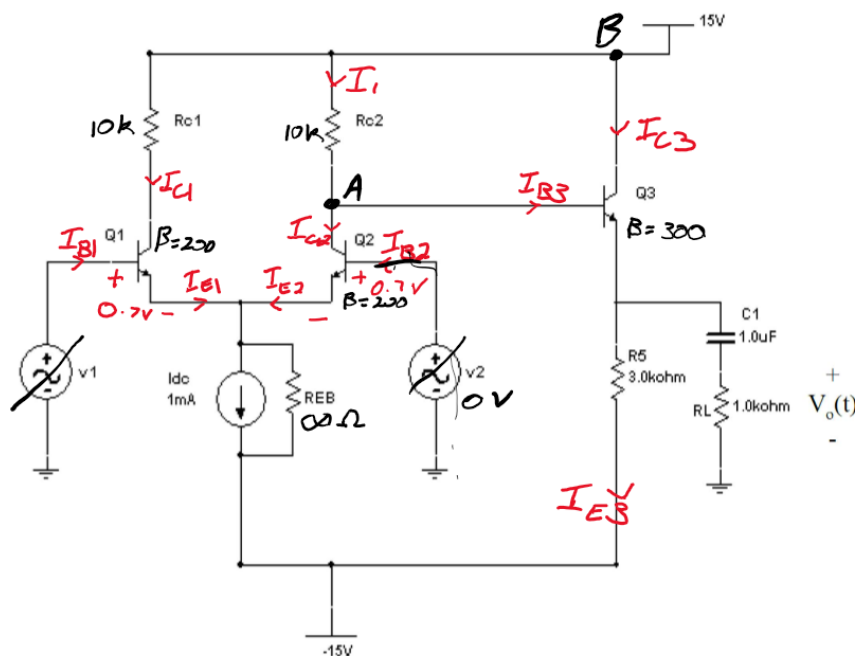


Figure 1: Circuit for Question 1

Calculating the DC operating points, first observe:

$$\text{As } V_{BE1} = V_{BE2} \Rightarrow I_{E1} = I_{E2}$$

\therefore KCL at current source:

$$I_{E1} + I_{E2} = 1 \text{ mA}$$

$$\therefore I_{E1} = I_{E2} = 0.5 \text{ mA}$$

And so follows:

$$I_{C1} = I_{C2} = \left(\frac{\beta}{\beta+1} \right) \times 0.5 \text{mA} \quad (\beta=200)$$
$$= 0.498 \text{mA}$$

We notice as β of $Q3$ is high,
 I_{B3} will be extremely small, thus
 $I_1 \approx I_{C2}$ thus

$$V_{B3} = 15 - I_{C2} \times 10000$$
$$= 10.02 \text{V}$$

thus Similarly:

$$V_{E3} = 10.02 - 0.7$$
$$= 9.32 \text{V}$$

And so: $I_{E3} = \frac{9.32 - (-15)}{3000}$

$$= 0.008 \text{A}$$
$$= 8 \text{mA}$$

Therefore we can conclude:

Q_1 :

$$V_C = 15 - 10000 I_{C1} = 10.02 \text{V}$$

$$V_B = 0 \text{V}$$

$$V_E = -0.7 \text{V}$$

$$I_C = 0.498 \text{mA}$$

Q_2 :

$$V_C = 15 - 10000 I_1 = 10.02 \text{V}$$

$$V_B = 0 \text{V}$$

$$V_E = -0.7 \text{V}$$

$$I_C = 0.498 \text{mA}$$

Q_3

$$V_C = 15 \text{V}$$

$$V_B = V_{C2} = 10.02$$

$$V_E = V_B - 0.7 = 9.32 \text{V}$$

$$I_C = I_E \times \left(\frac{\beta}{\beta+1} \right) \approx 8 \text{mA}$$

If $R_{EB} = 470k\Omega$

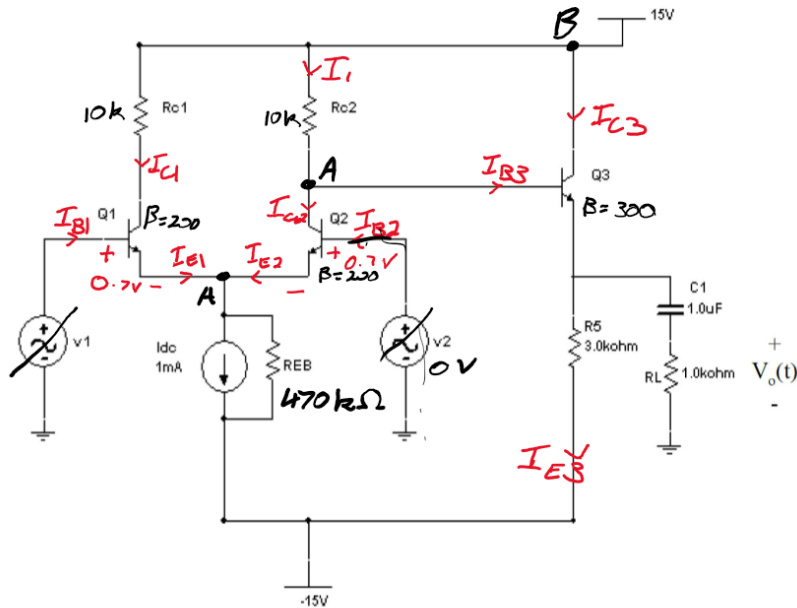


Figure 1: Circuit for Question 1

We understand

$$V_{REB} = \frac{-0.7 - (-15)}{470k\Omega} = 0.03mA$$

Thus KCL at A:

$$I_{E1} + I_{E2} = 1mA + 0.03mA$$

$$I_{E1} = I_{E2} = 0.5mA$$

$$\therefore I_{C1} = I_{C2} = 0.5mA \times \left(\frac{200}{201}\right) = 0.498mA$$

Thus as Q3 is large

$$V_{C1} \approx V_{C2} \approx 15 - 0.498 \times 10^{-3} \times 10000 = 10.02V$$

And so again:

Q_1 :

$$V_C = 15 - 10000 I_{C1} = 10.02V$$

$$V_B = 0V$$

$$V_E = -0.7V$$

$$I_C = 0.498mA$$

Q_2 :

$$V_C = 15 - 10000 I_{C2} = 10.02V$$

$$V_B = 0V$$

$$V_E = -0.7V$$

$$I_C = 0.498mA$$

Q_3

$$V_C = 15V$$


$$V_B = V_{C2} = 10.02$$

$$V_E = V_B - 0.7 = 9.32V$$

$$I_C = I_E \times \left(\frac{\beta}{\beta+1}\right) \approx 8mA$$

As for both $R_{EB} = \infty$
and $R_{EB} = 470k\Omega$ $V_C > V_B > V_E$,
we understand all the transistors
are in the active region.

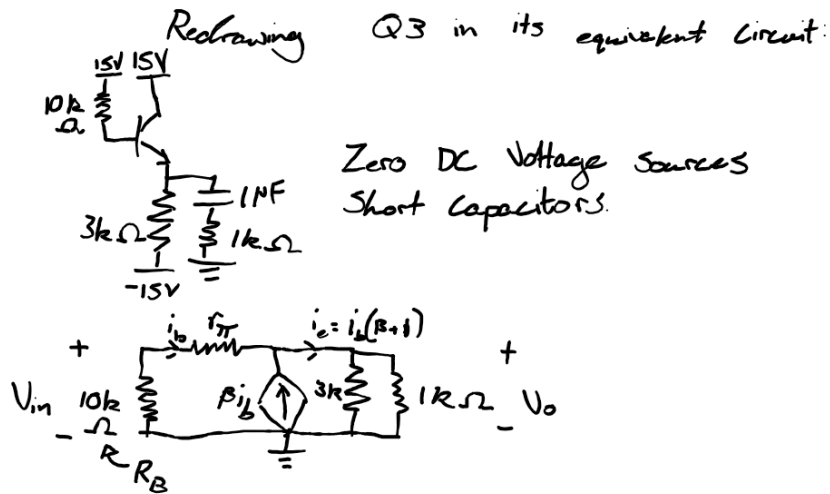- (b) Draw the mid-band small signal equivalent circuit of the common-collector stage (Q3), taking the load R_L into account. Derive symbolic expressions for the input impedance Z_{in} and the voltage gain A_v of the common collector (CC) stage. Substitute values for circuit components as given in Figure 1 and calculate numerical figures for Z_{in} and A_v .



$$R_L \parallel R_E = \frac{3 \times 1}{3+1} \text{ k}\Omega = 750 \Omega$$

Thus $V_o = 750 \times i_b(\beta+1)$

KVL: $V_{in} = i_b r_{\pi} + i_b(\beta+1) \times 750$

$$\therefore \frac{V_{in}}{V_o} = \frac{(1+\beta) \times 750}{r_{\pi} + (1+\beta) \times 750}$$

given $\beta = 300$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{300 \times 0.026}{8 \text{ mA}} = 975 \Omega$$

$$\therefore \frac{V_o}{V_{in}} = A_v = 0.996$$


We also know:

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{i_{B3} (r_{\pi 3} + R_E(\beta+1))}{i_{B3}}$$

$$= r_{\pi 3} + R_E(\beta+1) = 226713 \Omega$$

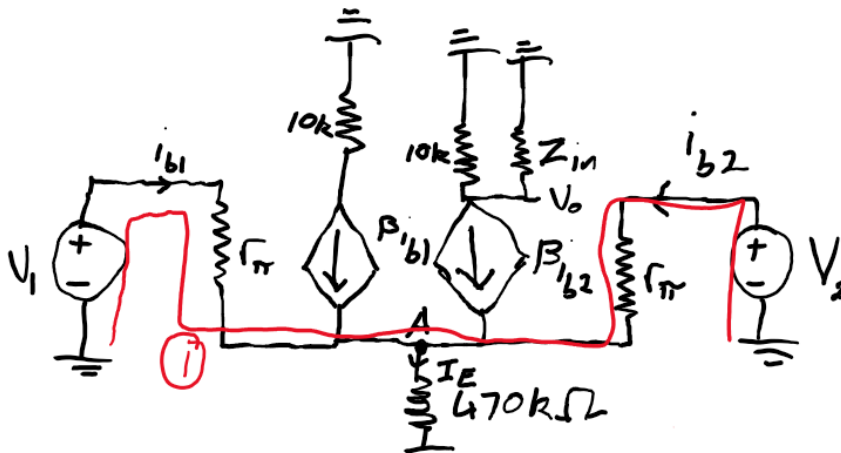- (c) Draw the differential mode half circuit of the amplifier in Figure 1, and derive an expression for the differential mode voltage gain (A_{vds}) of the differential amplifier stage, i.e., gain from the differential-mode input to the collector of Q2. The loading effect from the amplifier formed by Q3 should be taken into account. $R_{c1} = R_{c2} = 10\text{ k}\Omega$ and $R_{EB} = 470\text{ k}\Omega$. Calculate A_{vds} .
- (c) Draw the differential mode half circuit of the amplifier in Figure 1, and derive an expression for the differential mode voltage gain (A_{vds}) of the differential amplifier stage, i.e., gain from the differential-mode input to the collector of Q2. The loading effect from the amplifier formed by Q3 should be taken into account. $R_{c1} = R_{c2} = 10\text{ k}\Omega$ and $R_{EB} = 470\text{ k}\Omega$. Calculate A_{vds} .


In differential mode: $V_{dm} = V_1 - V_2$
 and thus $V_o = -V_1 = \frac{V_{dm}}{2}$



We first notice $I_E = 0$ as the emitter symmetry and equal yet opposite V_1 and V_2 polarities means the currents are equal.



We notice the following half circuit:

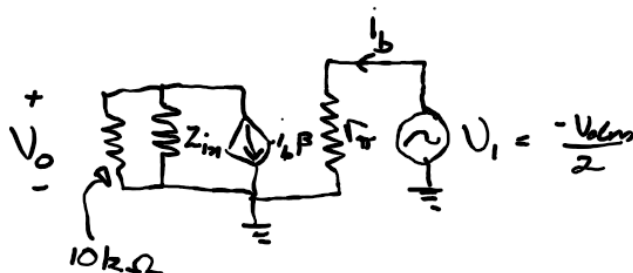

$$0 = i_{b1}(1+\beta) + i_{b2}(1+\beta)$$

$$\therefore i_{b1} = -i_{b2}$$

Sub into ①

$$V_1 - V_2 = r_{\pi}(-2i_{b2})$$

Notice:

$$V_o = -\beta i_{b2} (10k \parallel Z_{in})$$

Thus

$$A_d = \frac{V_o}{V_1 - V_2} = \frac{-\beta i_{b2} (10k \parallel Z_{in})}{-2 r_{\pi} i_{b2}}$$

$$r_{\pi} = \frac{200 \times 0.026}{0.498 \times 10^{-3}} = 10441.8 \Omega$$

$$10k \parallel Z_{in} = 9577.5 \Omega$$

Thus:

$$A_d = 91.7$$

- (d) The common-mode voltage gain from the common-mode input to the collector of Q2 has been calculated to be $A_{vcm} = -0.01$. The two components $v_{sig}(t)$ and $v_{unw}(t)$ appear at the two inputs $v_1(t)$ and $v_2(t)$ of the amplifier as described by Eq. (1) and (2):

$$v_1(t) = v_{sig}(t) + v_{unw}(t) \quad (1)$$

$$v_2(t) = 0.01 v_{sig}(t) + 0.99 v_{unw}(t) \quad (2)$$

Write an expression for the voltage at the collector of Q2, when signals $v_1(t)$ and $v_2(t)$ are applied as shown in Figure 1. Has the amplifier succeeded in selectively amplifying the signal of interest $v_{sig}(t)$?

$$V_{vcm} = -0.01$$

$$V_1(t) = V_{sig}(t) + V_{unw}(t)$$

$$V_2(t) = 0.01 V_{sig}(t) + 0.99 V_{unw}(t)$$

We know the total amplification to be:

$$V_o(t) = A_{dm} V_{dm} + A_{cm} V_{cm}$$

$$V_{dm} = V_1(t) - V_2(t) = 0.99 V_{sig}(t) + 0.01 V_{unw}(t)$$

$$V_{cm} = \frac{V_1 + V_2}{2} = \frac{1.01}{2} V_{sig}(t) + \frac{1.99}{2} V_{unw}(t)$$

$$V_o(t) = 91.7 \times 0.99 V_{sig} + 91.7 \times 0.01 V_{unw} - 0.01 \times \frac{1.01}{2} V_{sig} - 0.01 \times \frac{1.99}{2} V_{unw}$$

$$= 90.78 V_{sig}(t) + 0.91 V_{unw}$$

By observation we notice $V_{sig}(t)$ was amplified by a factor of 90.78, whilst V_{unw} was reduced by a factor of 0.91.



We can further describe this relationship by observing the common-mode rejection ratio:

$$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|} = 79.24 \text{ dB}$$

This lies within the typical low frequency CMRR range of 70dB to 100dB, indicating it was very successful at amplifying the $V_{sig}(t)$ signal.

2. (40 marks)

Figure 2 (a) shows a BJT cascode amplifier with a cascode active load. Figure 2 (b) is the corresponding small signal equivalent circuit for Q1 and Q2 in Figure 2 (a). The transistor parameters are $\beta = 120$ and $V_A = 80$ V. Assume $g_m \gg \frac{1}{r_o}$, $V_T = 0.026$ V. The V_{BB} voltage is such that all transistors are biased in the active region. Determine the small signal voltage gain $A_v = \frac{v_o}{v_i}$.

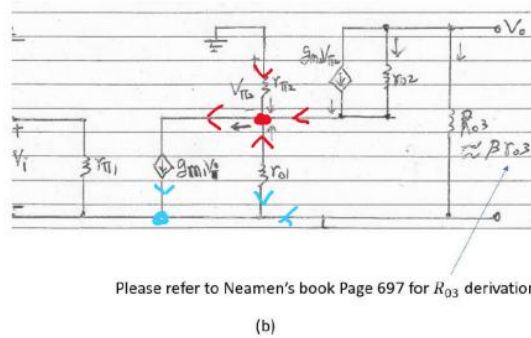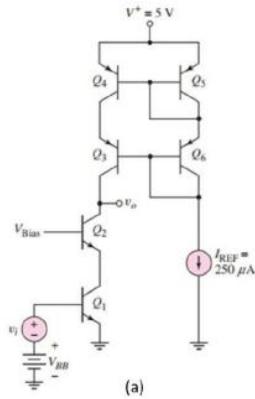

Beginning with diagram b:

KCL at red:

$$g_{m1} V_i = \frac{V_{\pi 2}}{r_{\pi 2}} + \frac{V_{r2}}{r_{o1}} + g_{m2} V_{r2} + \frac{V_o - V_{r2}}{r_{o2}}$$

KCL at Blue:

$$\frac{V_o}{R_{o3}} + \frac{V_o - V_{r2}}{r_{o2}} + g_{m2} V_{r2} = 0$$

$$g_{m1} V_i = V_{r2} \left(\frac{1}{r_{\pi 2}} + \frac{1}{r_{o1}} + g_{m2} + \frac{1}{r_{o2}} \right) + \frac{V_o}{r_{o2}}$$

$$V_o \left(\frac{1}{R_{o3}} + \frac{1}{r_{o2}} \right) + V_{r2} \left(\frac{1}{r_{o2}} + g_{m2} \right) = 0$$


given $g_m \gg \frac{1}{r_o}$

$$g_{m1} V_i = V_{r2} \left(\frac{1+\beta}{r_{\pi 2}} \right) + \frac{V_o}{r_{o2}} \quad (1)$$

$$V_o \left(\frac{1}{R_{o3}} + \frac{1}{r_{o2}} \right) + V_{\pi 2} g_{m2} = 0$$

$$V_{\pi 2} = -\frac{V_o}{g_{m2}} \left(\frac{1}{R_{o3}} + \frac{1}{r_{o2}} \right)$$

Subbing $V_{\pi 2}$ into ①

$$g_{m1} V_i = -\frac{V_o}{g_{m2}} \left(\frac{1}{R_{o3}} + \frac{1}{r_{o2}} \right) \left(\frac{1+\beta}{r_{\pi 2}} \right) + \frac{V_o}{r_{o2}}$$


Notice $g_{m2} \times r_{\pi 2} = \beta$

$$g_{m1} V_i = -V_o \left(\left(\frac{1}{R_{o3}} + \frac{1}{r_{o2}} \right) \left(\frac{1+\beta}{\beta} \right) + \frac{1}{r_{o2}} \right)$$

Given r_{o2} is so small:

$$g_{m1} V_i \approx -\frac{V_o}{R_{o3}} \left(\frac{1+\beta}{\beta} \right)$$

$$\frac{V_o}{V_i} = -g_{m1} R_{o3} \left(\frac{\beta}{\beta+1} \right)$$

Which gives $R_o \approx \beta r_{o3}$

$$\frac{V_o}{V_i} = \frac{-g_{m1} r_{o3} \beta^2}{1+\beta}$$

We now make the assumption that the base currents of the transistors are very small. Given the transistors are all of equal β , from KCL we find $I_{E6} \approx I_{C6} = I_{E5} \approx I_{C5}$ and so on. Following this we can justify $I_{C1} \approx I_{REF}$

Our understanding g_{m1} is given by:

$$g_{m1} = \frac{I_{REF}}{V_T} = \frac{250 \times 10^{-3}}{0.026} = 9.62 \frac{\text{mA}}{\text{V}}$$

$$\text{and } r_{o3} = \frac{V_A}{I_{REF}} = 320 \text{ K}$$

$$\begin{aligned} \therefore \frac{V_o}{V_i} = A_v &= \frac{-9.615 \times 320 \times 120^2}{121} \\ &= -366164.63 \end{aligned}$$