



As it is an ideal op amp, we understand  
 $V_- = V_+$  thus:

$$V_A = V_g \frac{Z_I}{Z_I + \cancel{80\Omega} R_1} \quad \text{where } R_1 = \cancel{10\text{mH}} 80\Omega$$

$$Z_I = (10 \times 10^{-3}) \omega j$$

Further, KCL at A we understand no  
 current passes through the op amp:

$$i_1 = i_2: \quad \frac{V_A}{R_2} = \frac{V_A - V_0}{Z_C \parallel R_3} \quad \text{where } R_2 = 5k\Omega$$

$$Z_C = j\omega(8 \times 10^{-9})$$

$$R_3 = 25k\Omega$$

Additionally we know  $V_- = V_0$  thus:

$$\frac{V_A}{R_2} = \frac{V_A - V_0}{Z_C \parallel R_3} \quad \text{thus: } V_g \left( \frac{Z_I}{Z_I + R_1} \right) = \frac{V_0}{Z_C \parallel R_3}$$

$$Z_C \parallel R_3 = \left( \frac{1}{Z_C} + \frac{1}{R_3} \right)^{-1} = \frac{Z_C R_3}{Z_C + R_3}$$

$$\text{Thus finally: } V_g \left( \frac{Z_I}{Z_I + R_1} \right) = V_g \left( \frac{Z_I}{Z_I + R_1} \right) \left( \frac{Z_C + R_3}{Z_C R_3} \right) - V_0 \left( \frac{Z_C + R_3}{Z_C R_3} \right)$$

$$\frac{V_0}{V_g} = \frac{\left( \frac{Z_I}{Z_I + R_1} \right) \left( \frac{Z_C + R_3}{Z_C R_3} \right) - \left( \frac{Z_I}{Z_I + R_1} \right)}{\frac{Z_C + R_3}{Z_C R_3}}$$



Subbing in these values we find:

$$\frac{V_g}{V_s} = \frac{1}{\left( \frac{10^{-2}j\omega}{10^{-2}j\omega + 80} \right) \left( \frac{25000 \frac{1}{8 \times 10^3 j\omega}}{\left( \frac{1}{8 \times 10^3 j\omega} + 25000 \right) \frac{1}{5 \times 10^3}} - 1 \right)}$$

$$= \left( 1 + \frac{80}{10^{-2}j\omega} \right) \left( \frac{25000}{\frac{1}{5 \times 10^3} + \frac{5}{8 \times 10^3 j\omega}} - 1 \right)^{-1}$$

$$= \frac{1 - \frac{8000j}{\omega}}{\frac{25000}{\frac{1}{5 \times 10^3} - \frac{625 \times 10^8}{\omega}} - 1}$$

Or alternatively:

$$\frac{V_o}{V_g} = \frac{\cancel{25000} \frac{25000}{(1/5 \times 10^3) - \frac{625 \times 10^8}{\omega}} - 1}{1 - \frac{8000j}{\omega}} = \left( \frac{(j\omega \times 10^{-2})}{8 \times 10^3 + j\omega} \right) \left( \frac{j\omega + 30000}{j\omega + 5000} \right)$$

Long simplification

Now given  $s = j\omega + \sigma$  we find for  $\sigma = 0$ :

$$\frac{V_o(s)}{V_g(s)} = \left( \frac{j\omega}{8 \times 10^3 + j\omega} \right) \left( \frac{j\omega + 30000}{j\omega + 5000} \right) = \frac{s(s + 30000)}{(s + 8000)(s + 5000)}$$

b) In order to change  $v_0(t)$  into a frequency dependent function, we use a Laplace transform.

$$\mathcal{L}\{0.6u(t)\} = 0.6 \mathcal{L}\{u(t)\}$$

which by definition  $= 0.6 \times \frac{1}{s} = V_0(s)$

Given  $\frac{V_0}{V_g}$  we find

$$\begin{aligned} V_0 &= \frac{V_g s(s+30000)}{(s+8000)(s+5000)} = \frac{0.6 s(s+30000)}{s(s+8000)(s+5000)} \\ &= \frac{0.6(s+30000)}{(s+8000)(s+5000)} \end{aligned}$$

Using partial fractions:

$$V_0 = \frac{A}{s+8000} + \frac{B}{s+5000}$$

We solve to find  $A = \frac{-22}{5}$  and  $B = 5$

$$\text{Thus finally } V_0 = \frac{-22}{5} \frac{1}{(s+8000)} + \frac{5}{(s+5000)}$$

With inverse Laplace  $\frac{k}{s+a} \rightarrow k e^{-at}$  from lectures

$$V_0(t) = \frac{-22}{5} e^{-8000t} + 5 e^{-5000t}$$



Q2)

Given we know the RLC will follow:  $i(t) = C \sin(\omega_c t) e^{-\alpha t}$   
and:

$$T \approx \frac{10.9 - 0.9}{8} = \frac{\text{First Peak} - \text{Second Peak}}{\text{Num. peaks}} = 1.255$$

we know since the graph follows  $\sin(\omega_c t)$ :

$$\omega_c = \frac{2\pi}{T} = \frac{2\pi}{1.25} = 5 \text{ rad/s}$$

We also see a decrease current factor:

$$\alpha = \frac{-\ln\left(\frac{A_{11}}{A_1}\right)}{t} = \frac{-\ln\left(\frac{0.2}{0.83}\right)}{10} = 0.143$$

Thus given:

$$L = \frac{R}{2\alpha} \quad \text{and} \Rightarrow L = \frac{100}{2 \times 0.14} = 351.4 \text{ H}$$

$$C = \frac{1}{L\omega_c^2} \quad \text{where} \quad \omega_0 = \sqrt{\omega_c^2 + \alpha^2} = \sqrt{5^2 + 0.14^2} = 5^{\text{th}} \text{ rad/s}$$

$$= \frac{1}{351.4 \times 5^2}$$

b) Ideally only power should be lost in resistor:

$$P = I^2 R = i(t)^2 R = A^2 e^{-2\alpha t} R$$

$$\begin{aligned} \text{Given } E_{(P_{\text{lost}})}(t) &= \int_0^t P_{\text{lost}} d\alpha = R \int_0^t A^2 e^{-2\alpha t} d\alpha \\ &= RA^2 \left[ \frac{1}{-2\alpha} e^{-2\alpha t} \right]_0^t = \frac{A^2 R}{-2\alpha} e^{-2t^2} + \frac{A^2 R}{2\alpha} \end{aligned}$$

And Finally, since  $E_{99\%} = 0.99 E_{\text{Initially}}$

we find

$$E_I = \lim_{t \rightarrow \infty} \left( \frac{A^2 R}{-2\alpha} e^{-2\alpha t} + \frac{A^2 R}{2\alpha} \right) = \frac{A^2 R}{2\alpha}$$

$$\text{we find: } E_{99\%} = 0.99 \frac{A^2 R}{2\alpha}$$

The time at which this occurs we then find by subbing it into our time varying equation:

$$0.99 \frac{A^2 R}{2\alpha} = \frac{A^2 R}{-2\alpha} e^{-2\alpha t} + \frac{A^2 R}{2\alpha}$$

$$t = 16.18 \text{ seconds}$$